



Project Report
CSE 231

Digital Logic Design
Section 11
Workstation-08

Using combinational circuit print: **SASJ-G08** in 7 segment display

Spring 2020
North South University
Submitted To: Tanjila Farah(TnF)

SL.	NAME :	Student ID :
1.	S M Gazzali Arafat Nishan	1831513642
2.	Rofiqul Alam Shehab	1831185042
3.	Sudipta Bhatta	1731194042

Index	A	B	C	a	b	c	d	e	f	g	
0	0	0	0	1	0	1	1	0	1	1	S
1	0	0	1	1	1	1	0	1	1	1	A
2	0	1	0	1	0	1	1	0	1	1	S
3	0	1	1	0	1	1	1	1	0	0	J
4	1	0	0	0	0	0	0	0	0	1	-
5	1	0	1	1	0	1	1	1	1	0	G
6	1	1	0	1	1	1	1	1	1	0	0
7	1	1	1	1	1	1	1	1	1	1	8

Generalized Functions:

$$a = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C \\ = \Sigma(0, 1, 2, 5, 6, 7)$$

$$b = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C = \Sigma(1, 3, 6, 7)$$

$$c = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + \\ ABC = \Sigma(0, 1, 2, 3, 5, 6, 7)$$

$$d = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C \\ = \Sigma(0, 2, 3, 5, 6, 7)$$

$$e = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + ABC \\ = \Sigma(1, 3, 5, 6, 7)$$

$$f = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$

$$\Sigma(0, 1, 2, 5, 6, 7)$$

$$g = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC$$

$$= \Sigma(0, 1, 2, 4, 7)$$

K-map for $a = f$

	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
A'	1	1	0	1
A	0	1	1	1

K-map for b

	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
A'	0	1	1	0
A	0	0	1	1

$$F = \bar{A}\bar{B} + \bar{B}C + AC + AB + B\bar{C}$$

$$F = A\bar{C} + AB$$

K-map for c

	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
A'	1	1	1	1
A	0	1	1	1

$$F = C + B + \bar{A}\bar{B} + A'\bar{C}'$$

K-map for d

	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
A'	1	0	1	1
A	0	1	1	1

$$F = B + AC + A'\bar{C}$$

K-map for c

	$B'C'$	$B'C$	BC	BC'
A'	0 0	1 1	1 3	0 2
A	0 4	1 5	1 7	1 6

$$F = c + AB$$

K-map for g

	$B'C'$	$B'C$	BC	BC'
A'	1 0	1 1	0 3	1 2
A	1 4	0 5	1 7	0 6

$$F = A'B' + B'C' + A'C' + ABc$$

✱ Simplification for sop

$$I) a = A'B' + B'C + AC + AB + B'C'$$

$$II) b = A'C + AB$$

$$III) c = c + B + A'B' + A'C'$$

$$IV) d = B + AC + A'C'$$

$$V) e = c + AB$$

$$VI) f = A'B' + B'C + AC + AB + B'C'$$

$$VII) g = A'B' + B'C' + A'C' + ABc$$

Generalized POS Function :

$$a = AB'C' + A'BC = (A' + B + C)(A + B' + C') = \pi(3, 4)$$

$$b = A'B'C' + A'BC' + AB'C' + ABC' = (A + B + C)(A + B' + C) \\ (A' + B + C)(A' + B' + C') = \pi(0, 2, 4, 6)$$

$$c = AB'C' = A' + B + C = \pi(4)$$

$$d = A'BC + AB'C' = (A + B + C')(A' + B + C) = \pi(1, 4)$$

$$e = A'B'C' + A'BC' + AB'C' = (A + B + C)(A + B' + C) \\ (A' + B + C) = \pi(0, 2, 4)$$

$$f = AB'C' + A'BC = (A' + B + C)(A + B' + C') = \pi(3, 4)$$

$$g = A'BC + AB'C + ABC' = (A + B' + C')(A' + B + C') \\ (A' + B' + C) = \pi(3, 5, 6)$$

k-map for $a = f$

	B'C'	B'C	BC	BC'
A'	1	1	0	1
A	0	1	1	1

$$F = (A + B' + C')(A' + B + C)$$

k-map for b

	B'C'	B'C	BC	BC'
A'	0	1	1	0
A	0	0	1	1

$$F = (A + C)(B + C)(A' + B)$$

K-map for c

	$B'C$	$B'C'$	BC	BC'
A'	1 0	1 1	1 3	1 2
A	0 4	1 5	1 7	1 6

$$F = A' + B + C$$

K-map for d

	$B'C$	$B'C'$	BC	BC'
A'	1 0	0 1	1 3	1 2
A	0 4	1 5	1 7	1 6

$$F = (A + B + C)(A' + B + C)$$

K-map for e

	$B'C$	$B'C'$	BC	BC'
A'	0 0	1 1	1 3	0 2
A	0 4	1 5	1 7	1 6

$$F = (A + C)(B + C)$$

K-map for g

	$B'C$	$B'C'$	BC	BC'
A'	1 0	1 1	0 3	1 2
A	1 4	0 5	1 7	0 6

$$F = (A + B' + C')(A' + B + C)(A' + B' + C)$$

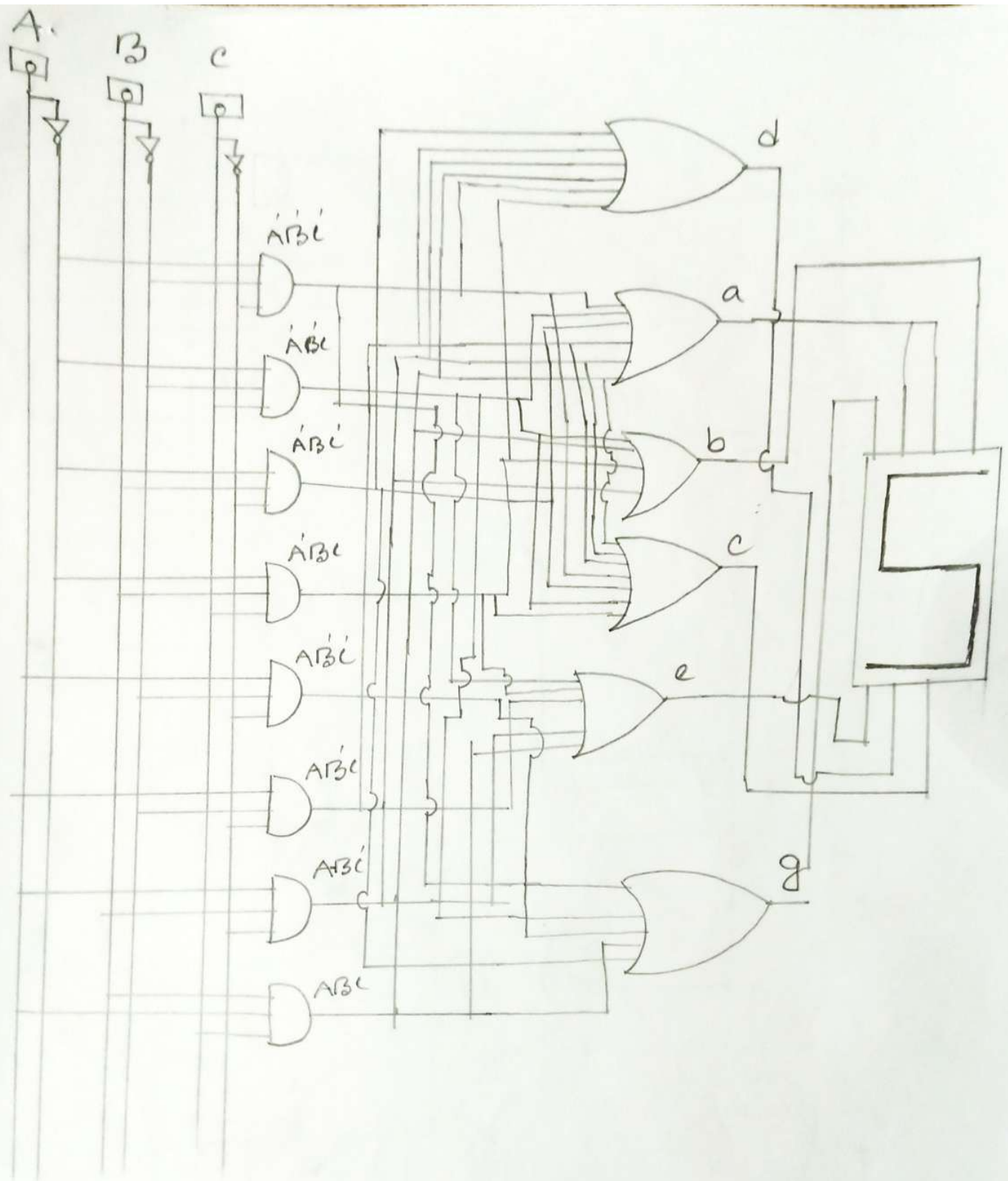


Fig: Generalized 80P Circuit Diagram Using Basic gates.

 


Fig: Simplified nop Circuit Diagram using basic gates.

 


Fig: Simplified SOP Circuit Diagram using NAND gates.

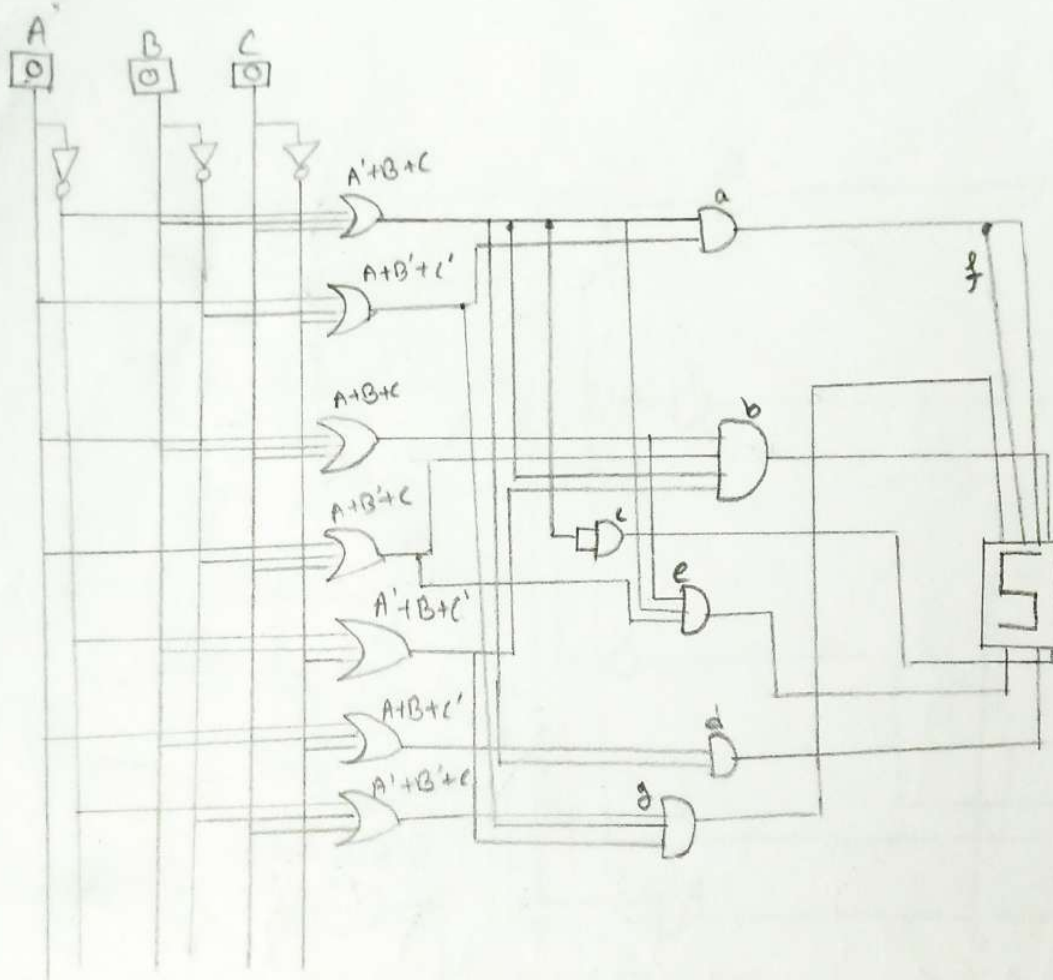


Fig: Generalized POS circuit diagram using logic gates.


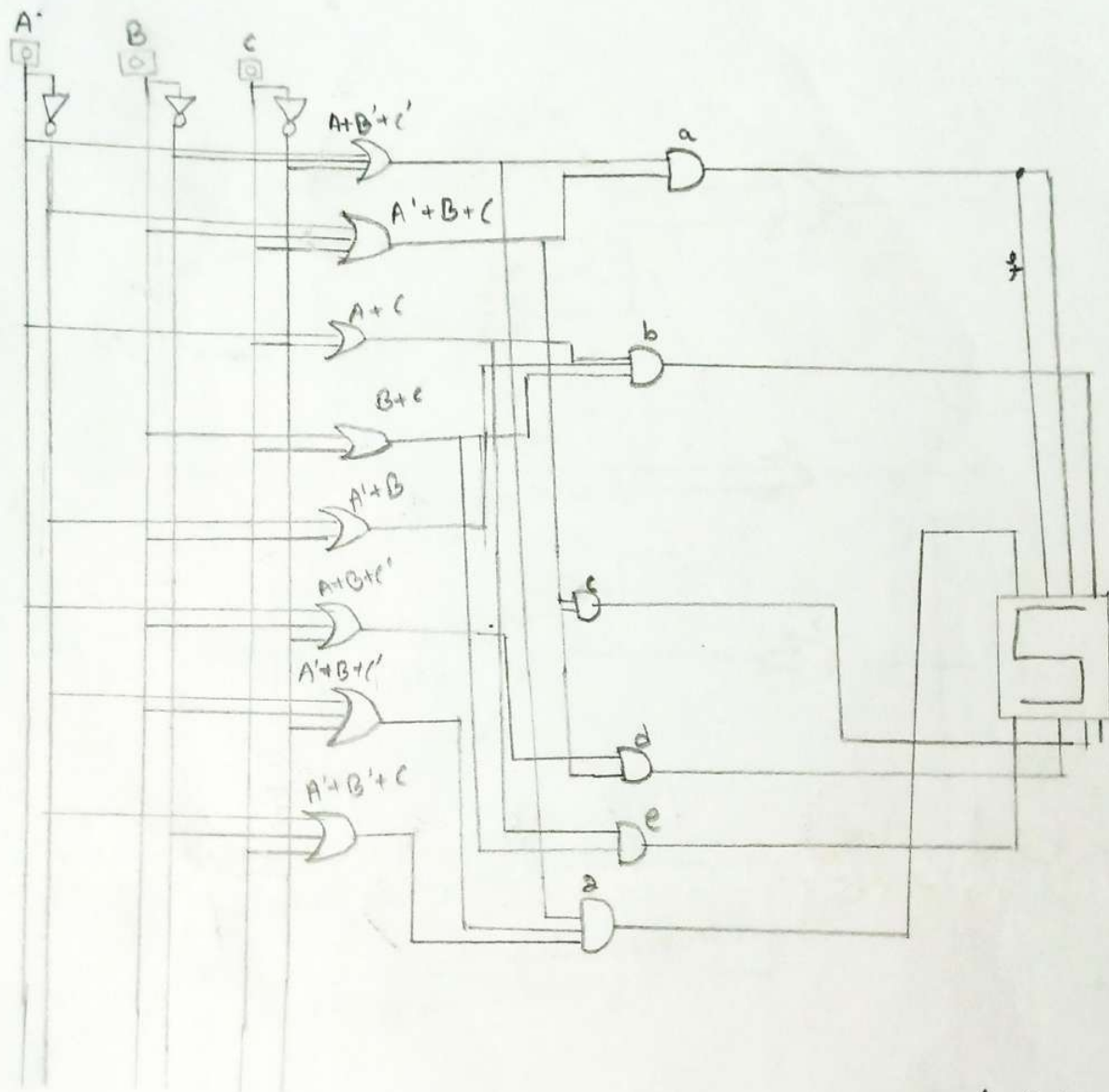


Fig: Simplified pos circuit Diagram
using basic gates

Fig: Simplified POS using only NOR gates

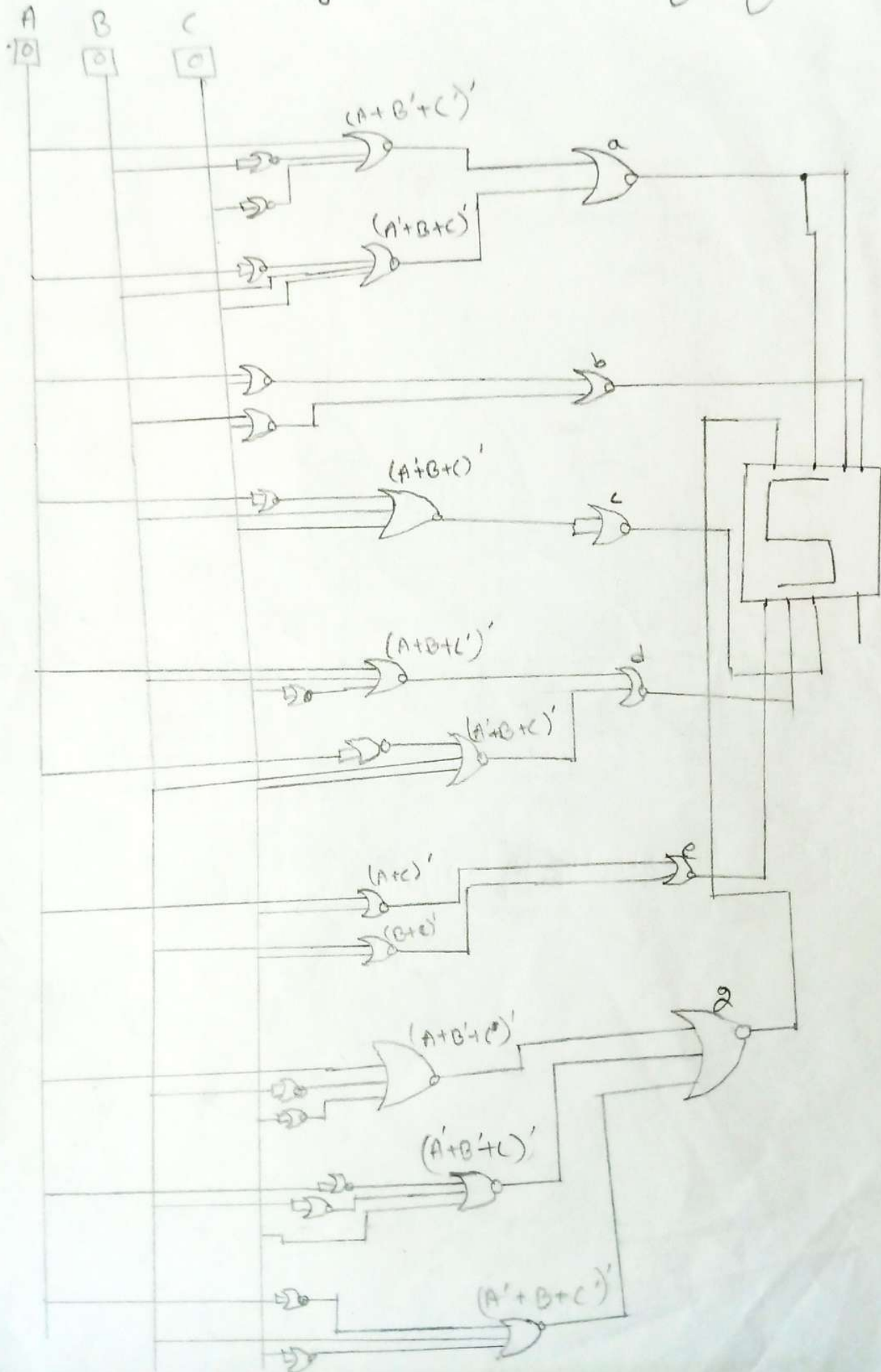


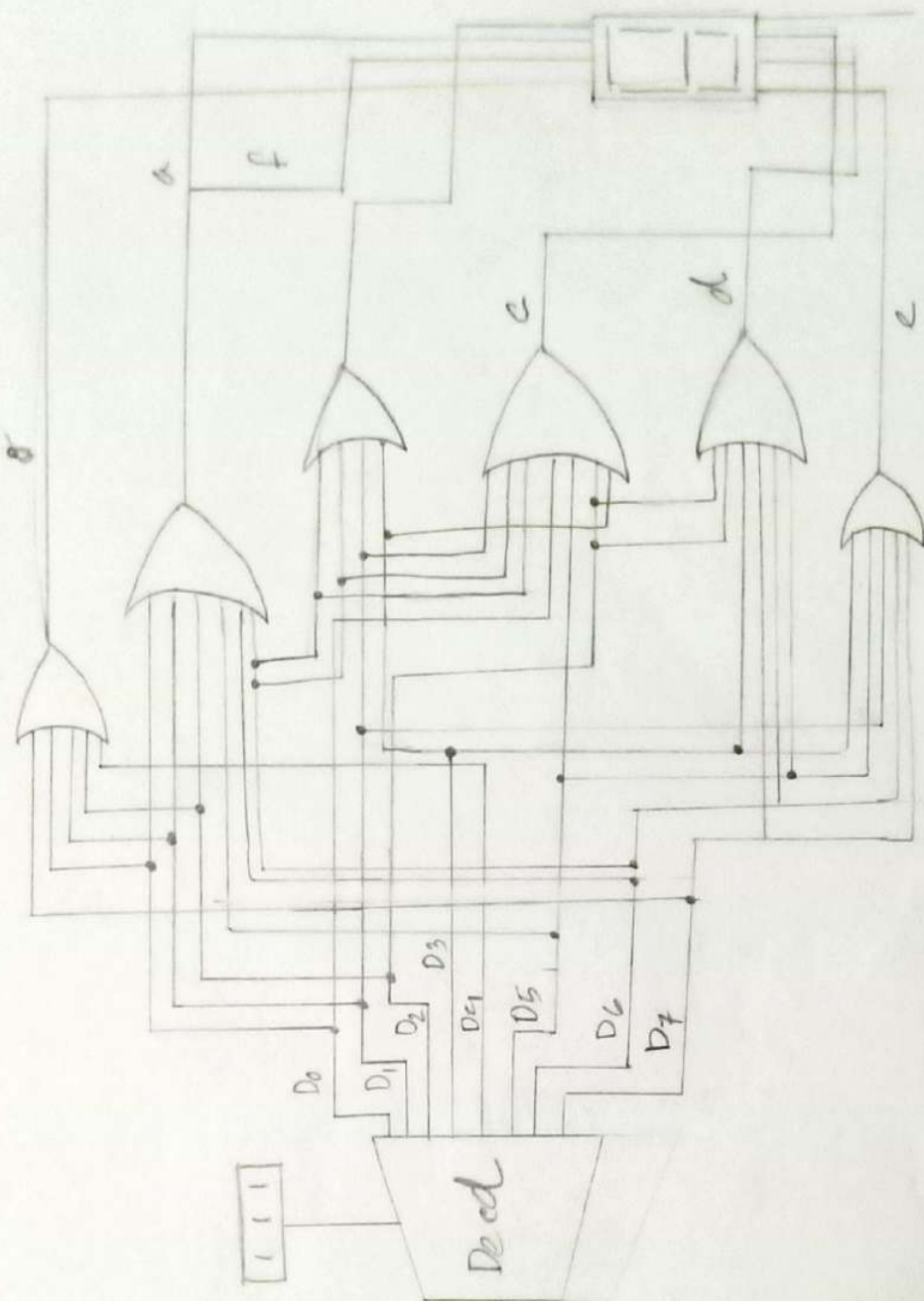


Fig: Generalized SOP Circuit Diagram using Decoder and

OR gate.

Fig: Generalized SOP Multiplexer

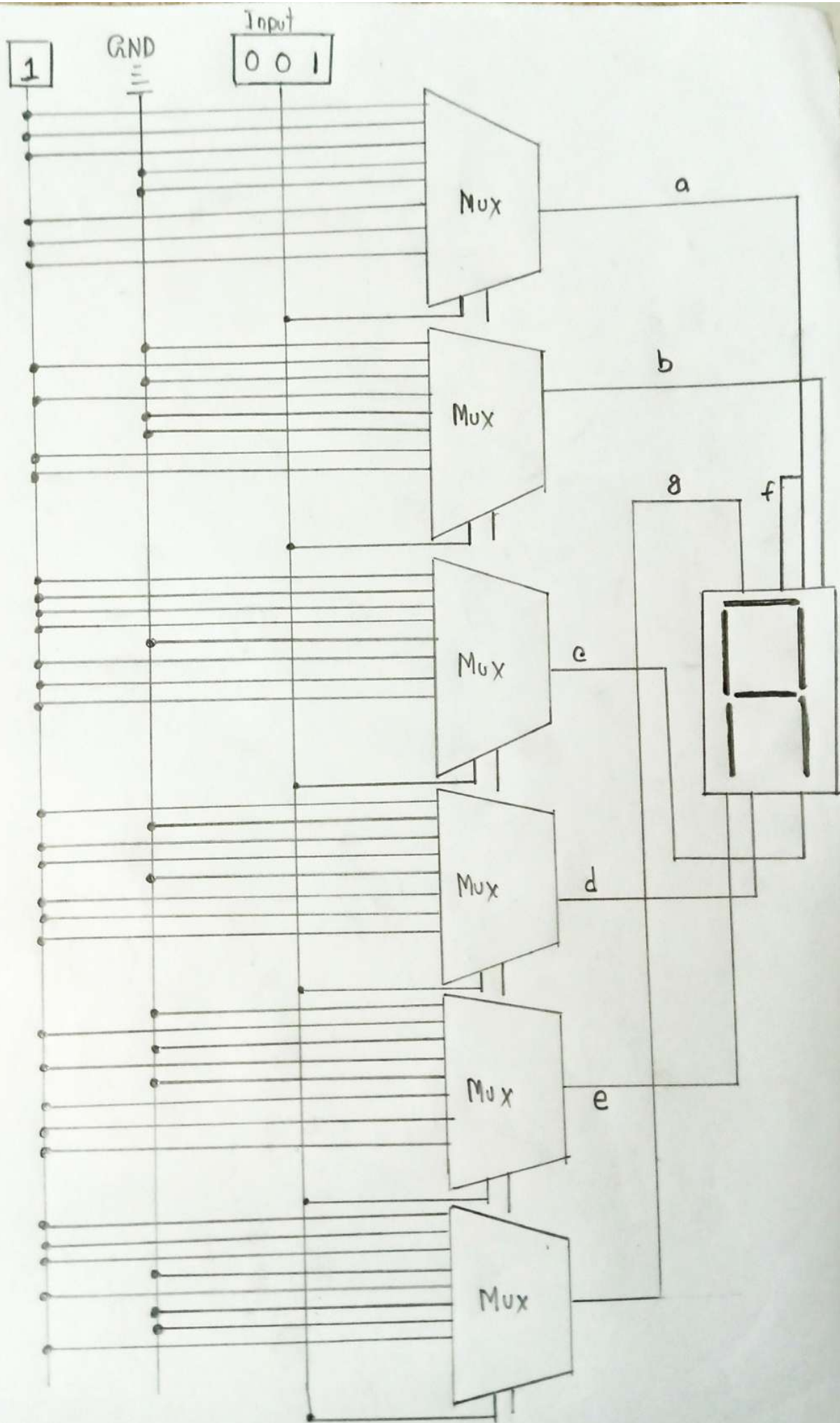

 


Fig. Circuit Diagram For Generalized SOP Equation

 


Fig. Project-Simplifeid SOP Circuit Diagram using basic gates

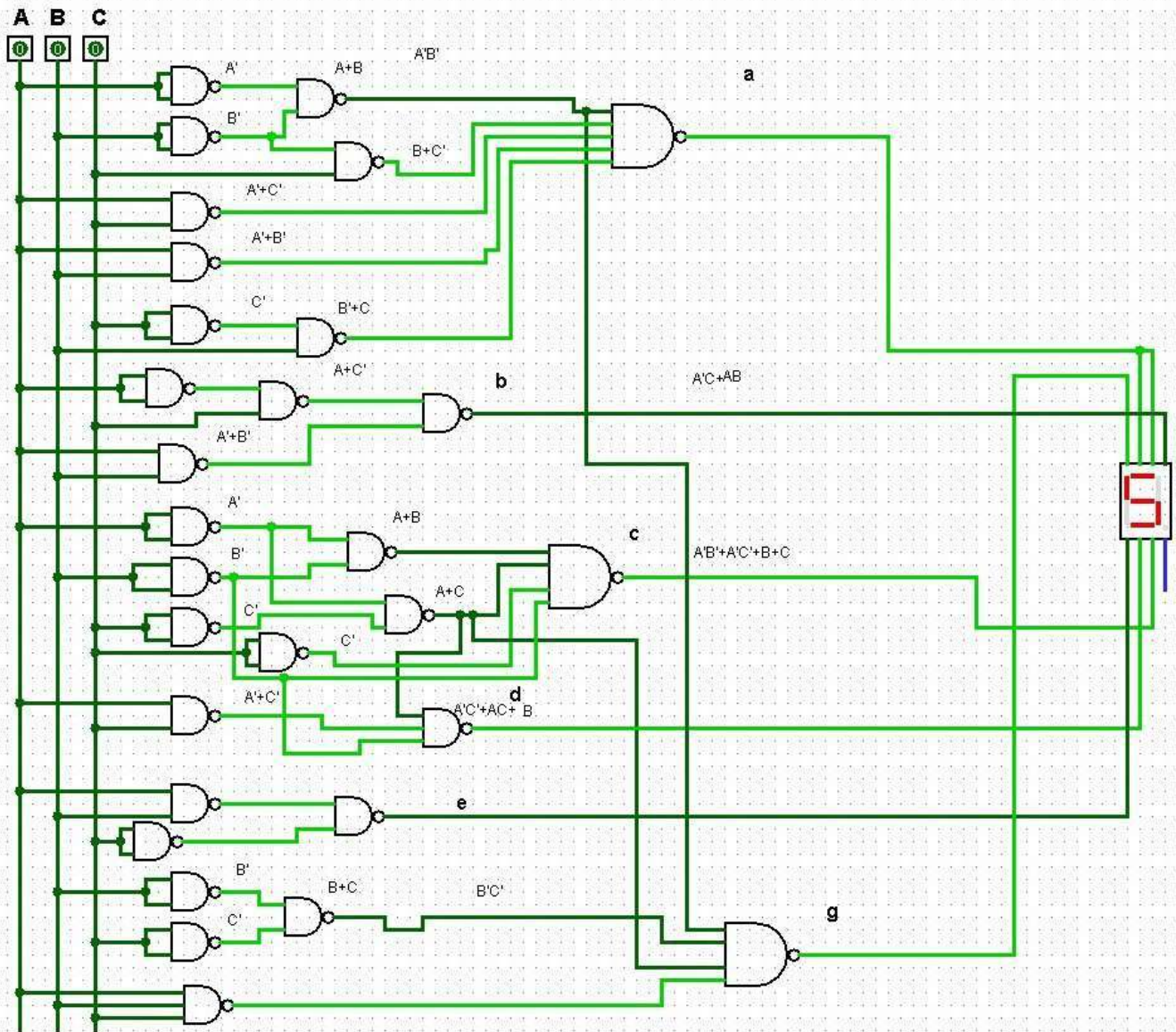


Fig. Circuit Diagram of SOP using only NAND Gates

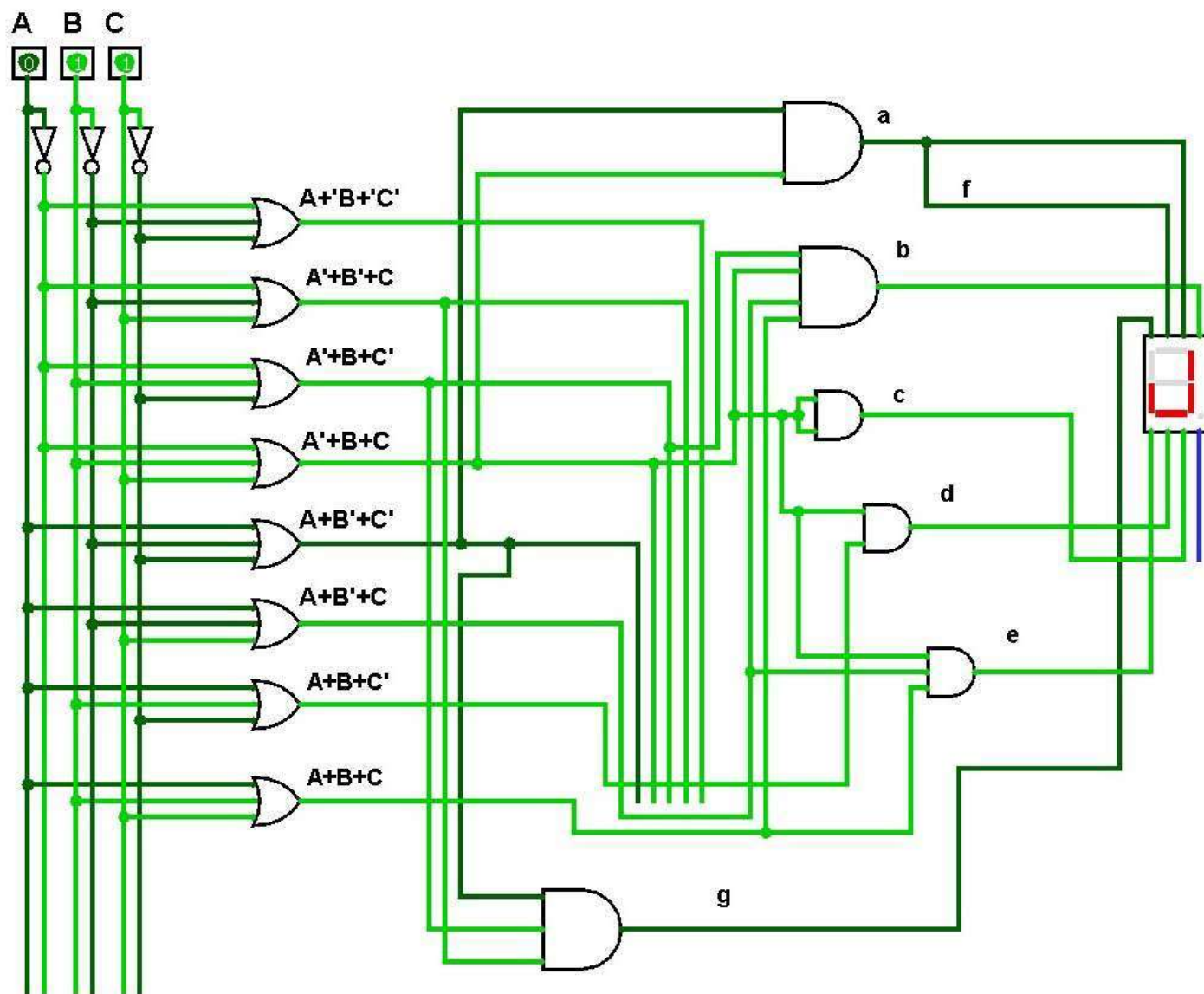


Fig. Circuit Diagram of Generalized POS

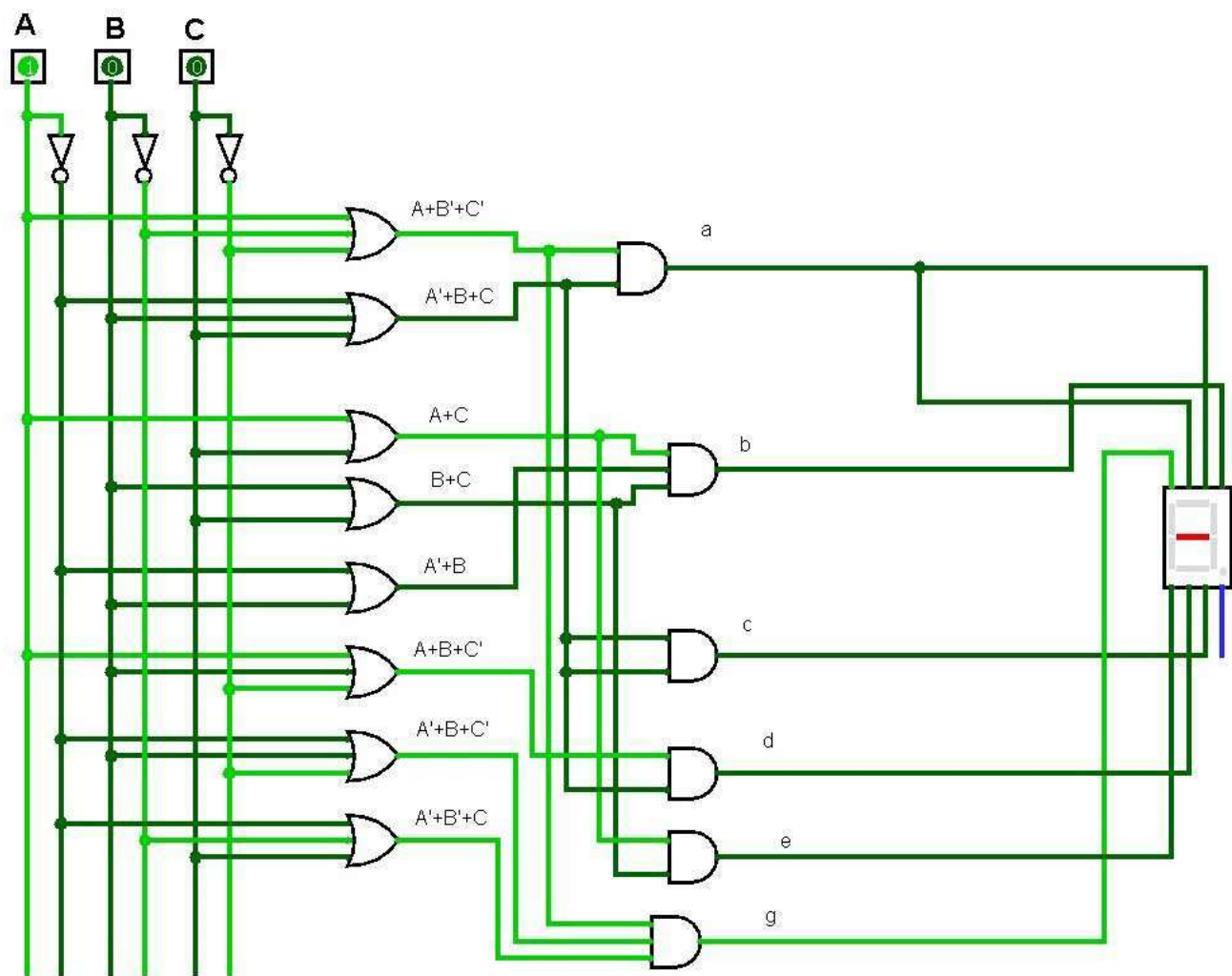


Fig.Circuit Diagram for Simplified POS Using Basic Gates

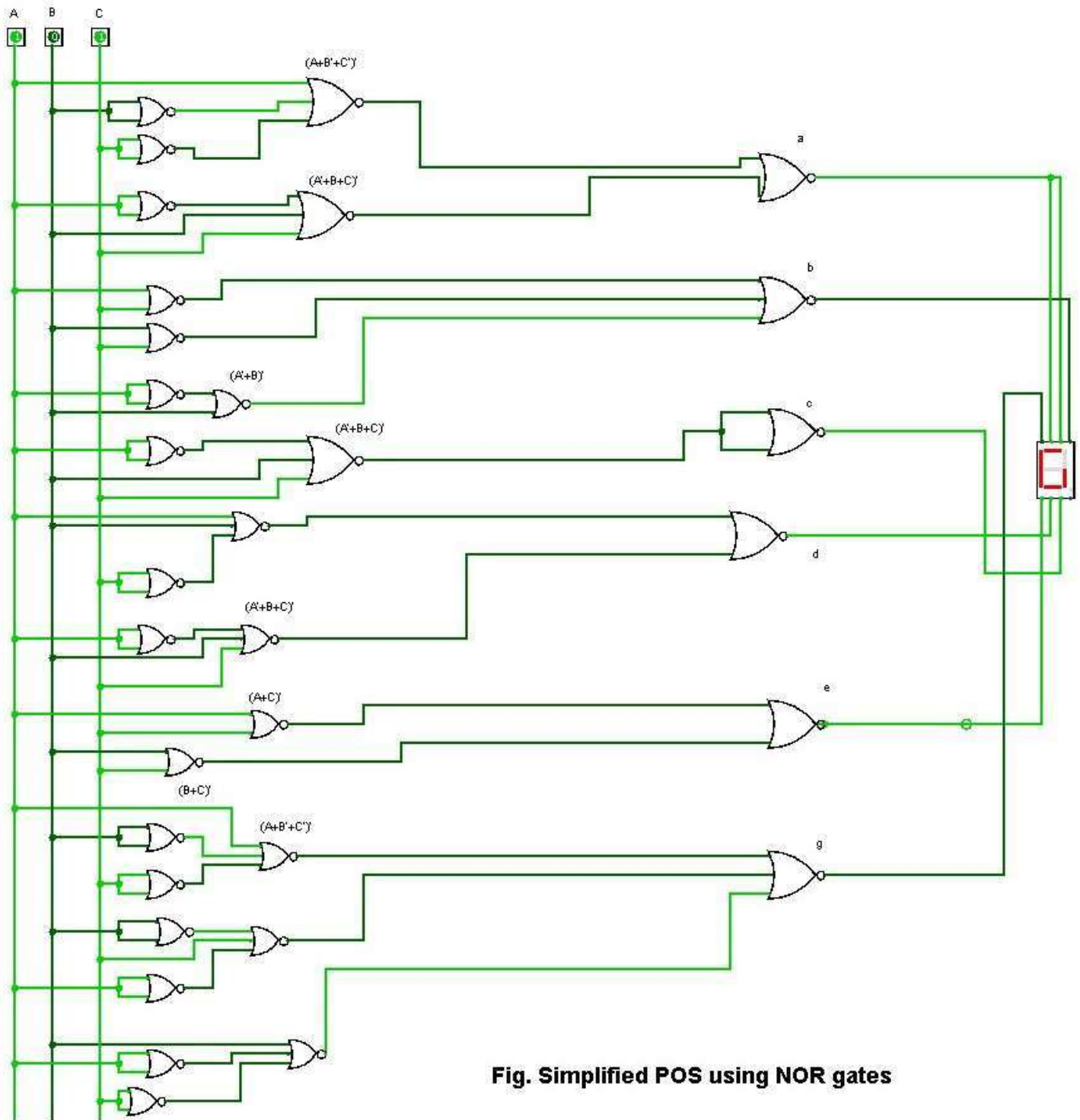


Fig. Simplified POS using NOR gates

 


Fig. Generalized SOP Using Decoder and OR Gates

