



Project Report
CSE 231

Digital Logic Design
Section 11
Workstation-08

Using combinational circuit print: SASJ-G08 in 7 segment display

Spring 2020
North South University
Submitted To: Tanjila Farah(TnF)

SL.	NAME :	Student ID :
1.	S M Gazzali Arafat Nishan	1831513642
2.	Rofiqul Alam Shehab	1831185042
3.	Sudipta Bhatta	1731194042

Index	A	B	C	a	b	c	d	e	f	g	
0	0	0	0	1	0	1	1	0	1	1	S
1	0	0	1	1	1	1	0	1	1	1	A
2	0	1	0	1	0	1	1	0	1	1	S
3	0	1	1	0	1	1	1	1	0	0	J
4	1	0	0	0	0	0	0	0	0	1	-
5	1	0	1	1	0	1	1	1	1	0	G
6	1	1	0	1	1	1	1	1	1	0	0
7	1	1	1	1	1	1	1	1	1	1	8

Generalized Functions:

$$a = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C \\ = \Sigma(0, 1, 2, 5, 6, 7)$$

$$b = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C = \Sigma(1, 3, 6, 7)$$

$$c = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + \\ ABC = \Sigma(0, 1, 2, 3, 5, 6, 7)$$

$$d = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC \\ = \Sigma(0, 2, 3, 5, 6, 7)$$

$$e = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + ABC \\ = \Sigma(1, 3, 5, 6, 7)$$

$$f = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + ABC$$

$$\Sigma(0,1,2,5,6,7)$$

$$g = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$= \Sigma(0,1,2,4,7)$$

K-map for $a = f$

	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
A'	1	1	0	1
A	0	1	1	1

$$F = \bar{A}\bar{B} + \bar{B}C + AC + AB + B\bar{C}$$

K-map for b

	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
A'	0	1	1	0
A	0	0	1	1

$$F = A\bar{C} + AB$$

K-map for c

	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
A'	1	1	1	1
A	0	1	1	1

$$F = C + B + \bar{A}\bar{B} + A\bar{C}$$

K-map for d

	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
A'	1	0	1	1
A	0	1	1	1

$$F = B + AC + A\bar{C}$$

K-map for e

	$B'C'$	$B'C$	BC	BC'
A'	0	1	1	0
A	0	1	1	1

$$F = C + AB$$

K-map for g

	$B'C'$	$B'C$	BC	BC'
A'	1	1	0	1
A	1	0	1	0

$$F = A'B + B'C' + A'C' + ABC$$

5. Simplification for sop

$$i) a = A'B + B'C + AC + AB + B'C'$$

$$ii) b = A'C + AB$$

$$iii) c = C + B + A'B + A'C'$$

$$iv) d = B + AC + A'C'$$

$$v) e = C + AB$$

$$vi) f = A'B + B'C + AC + AB + B'C'$$

$$vii) g = A'B + B'C' + A'C' + ABC$$

Generalized POS Function :

$$a = AB'C' + A'BC = (A+B+C)(A+B'+C) = \pi(3,4)$$

$$b = A'B'C' + A'BC' + AB'C' + ABC' = (A+B+C)(A+B'+C)(A'+B+C)(A'+B+C') = \pi(0,2,4,6)$$

$$c = AB'C' = A+B+C = \pi(4)$$

$$d = A'B'C + AB'C' = (A+B+C')(A'+B+C) = \pi(1,4)$$

$$e = A'B'C' + A'BC' + AB'C' = (A+B+C)(A+B'+C)(A'+B+C) = \pi(0,2,4)$$

$$f = AB'C' + A'BC = (A+B+C)(A+B'+C') = \pi(3,4)$$

$$g = A'BC + AB'C + ABC' = (A+B'+C')(A'+B+C')(A'+B'+C) = \pi(3,5,6)$$

k-map for $a=f$

	B'C'	B'C	BC	BC'
A'	1	1	0	1
A	0	1	1	1

$$F = (A+B+C')(A'+B+C)$$

k-map for b

	B'C'	B'C	BC	BC'
A'	0	1	1	0
A	0	0	1	1

$$F = (A+C)(B+C)(A'+B)$$

K-map for c

	$B'C$	$B'C$	BC	BC'
A'	1 0	1 1	1 3	1 2
A	0 4	1 5	1 7	1 6

$$F = A' + B + C$$

K-map for d

	$B'C$	$B'C$	BC	BC'
A'	1 0	0 1	1 3	1 2
A	0 4	1 5	1 7	1 6

$$F = (A + B + C)(A' + B + C)$$

K-map for e

	$B'C$	$B'C$	BC	BC'
A'	0 0	1 1	1 3	0 2
A	0 4	1 5	1 7	1 6

$$F = (A + C)(B + C)$$

K-map for g

	$B'C$	$B'C$	BC	BC'
A'	1 0	1 1	0 3	1 2
A	1 4	0 5	1 7	0 6

$$F = (A + B' + C')(A' + B + C)(A' + B' + C)$$

 


Fig: Generalized SOP Circuit Diagram Using Basic gates.

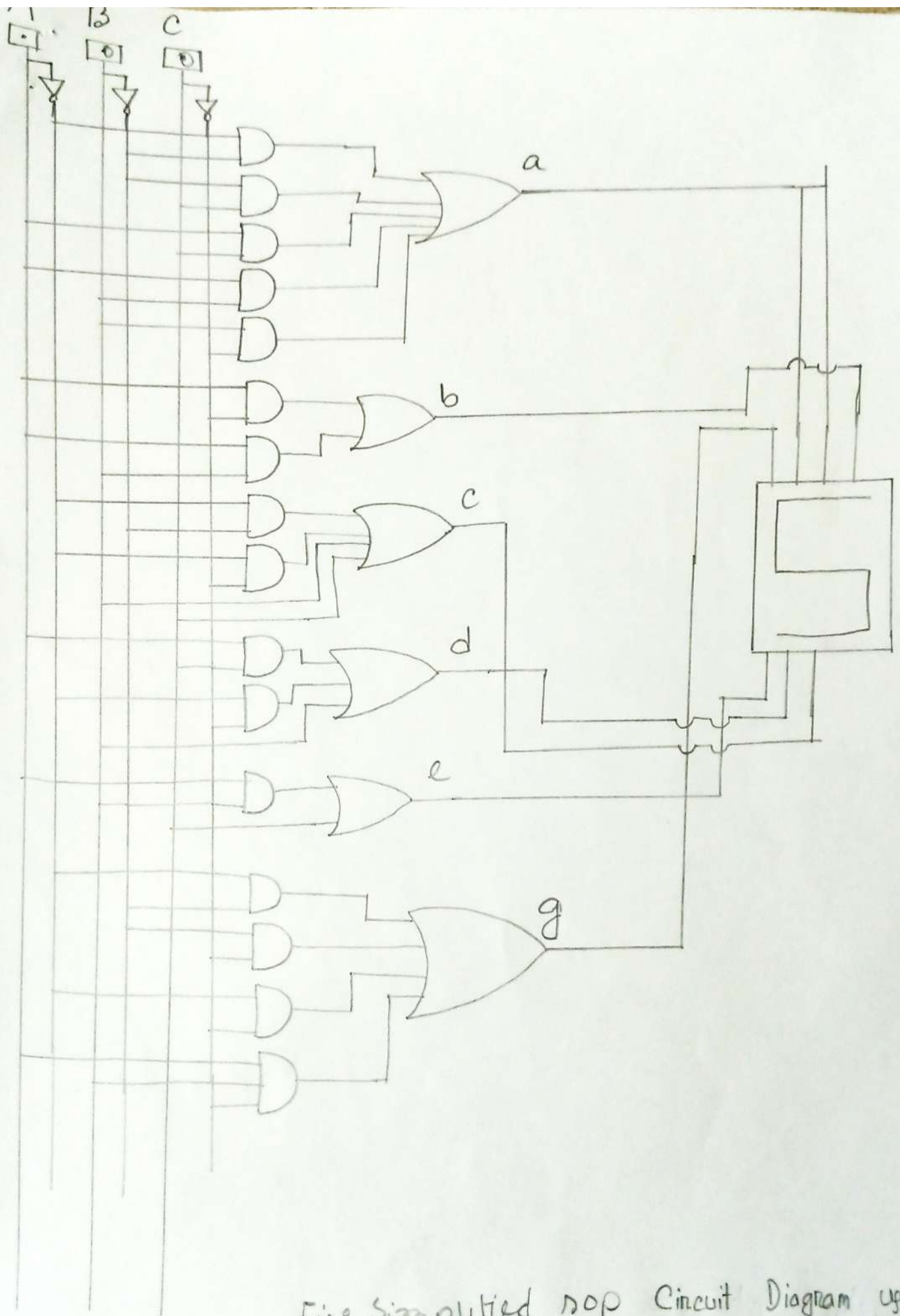


Fig: Simplified nop Circuit Diagram using basic gates.

 


Fig: Simplified SOP Circuit Diagram using NAND gates.

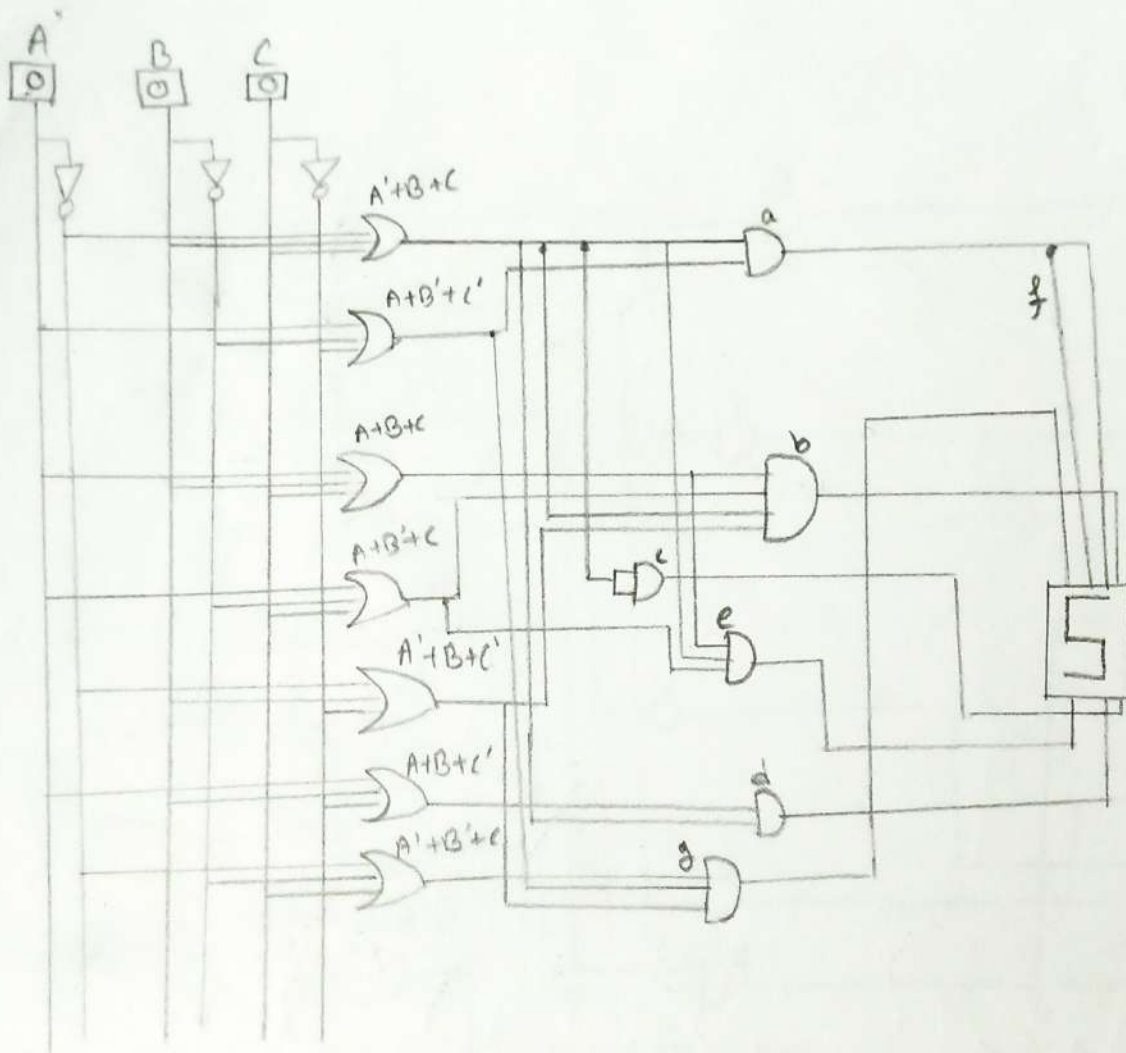


Fig: Generalized POS circuit diagram using basic gates.


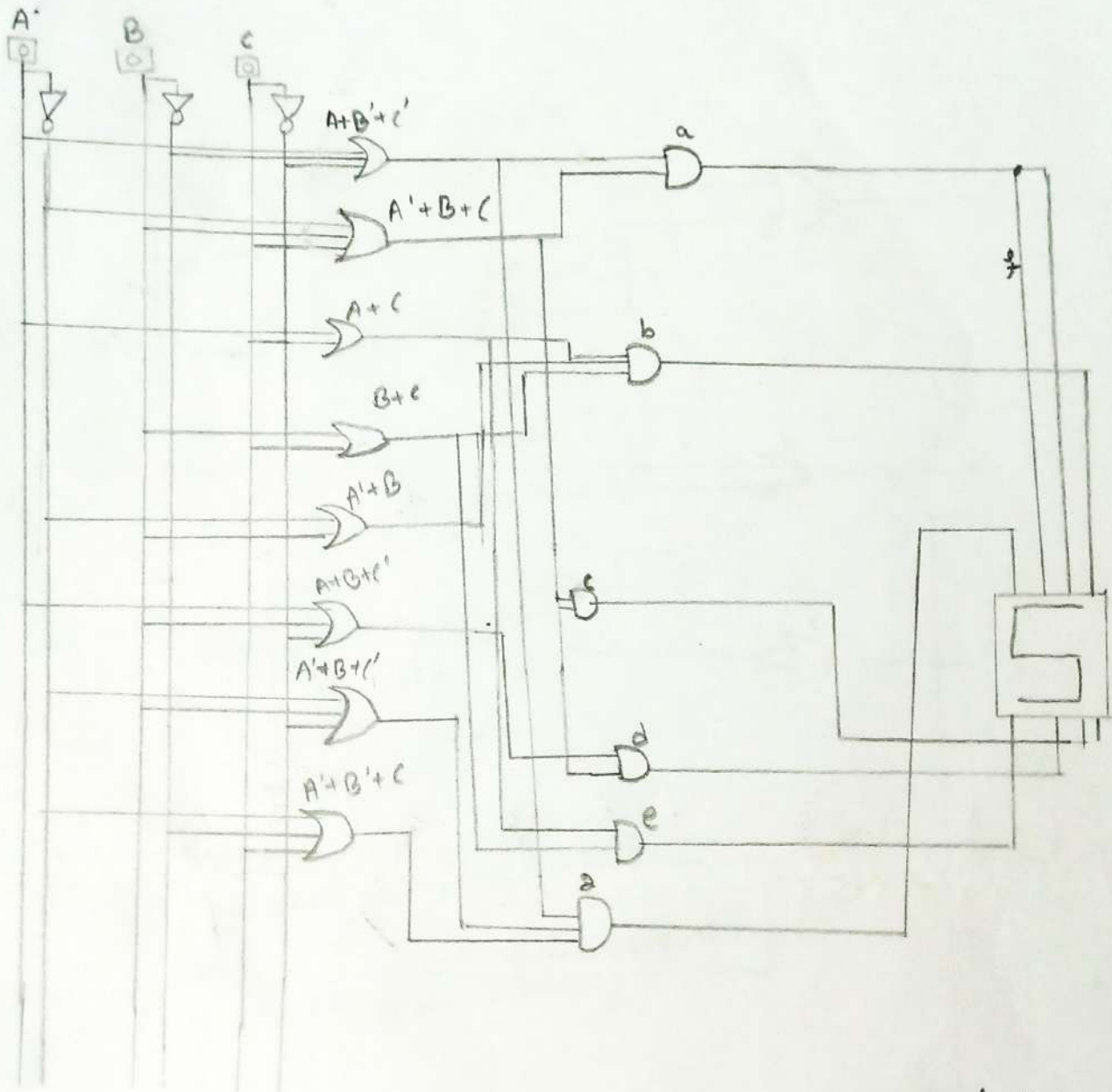


Fig. Simplified pos circuit Diagram
using basic gates

Fig: Simplified POS using only NOR gates

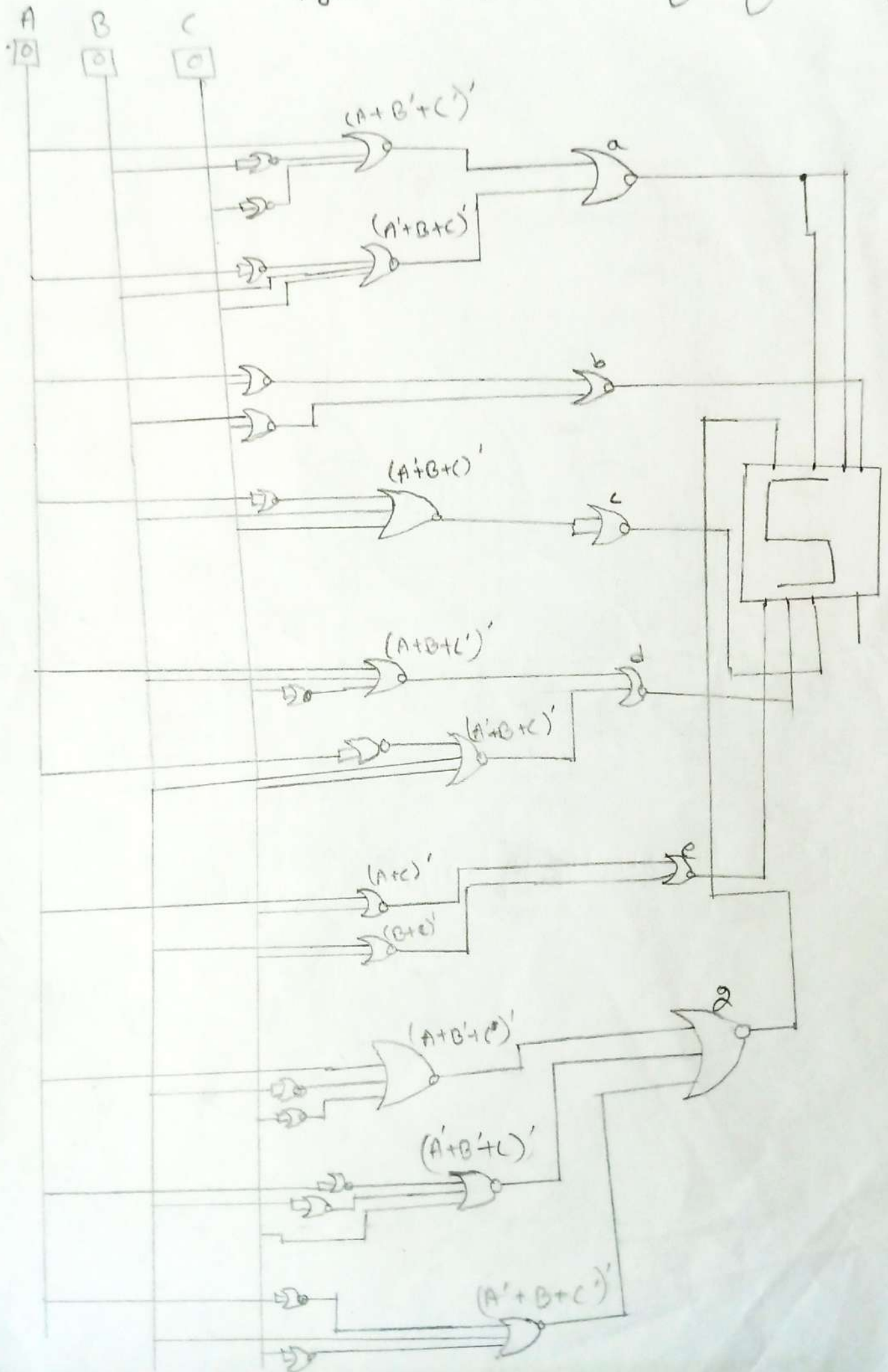


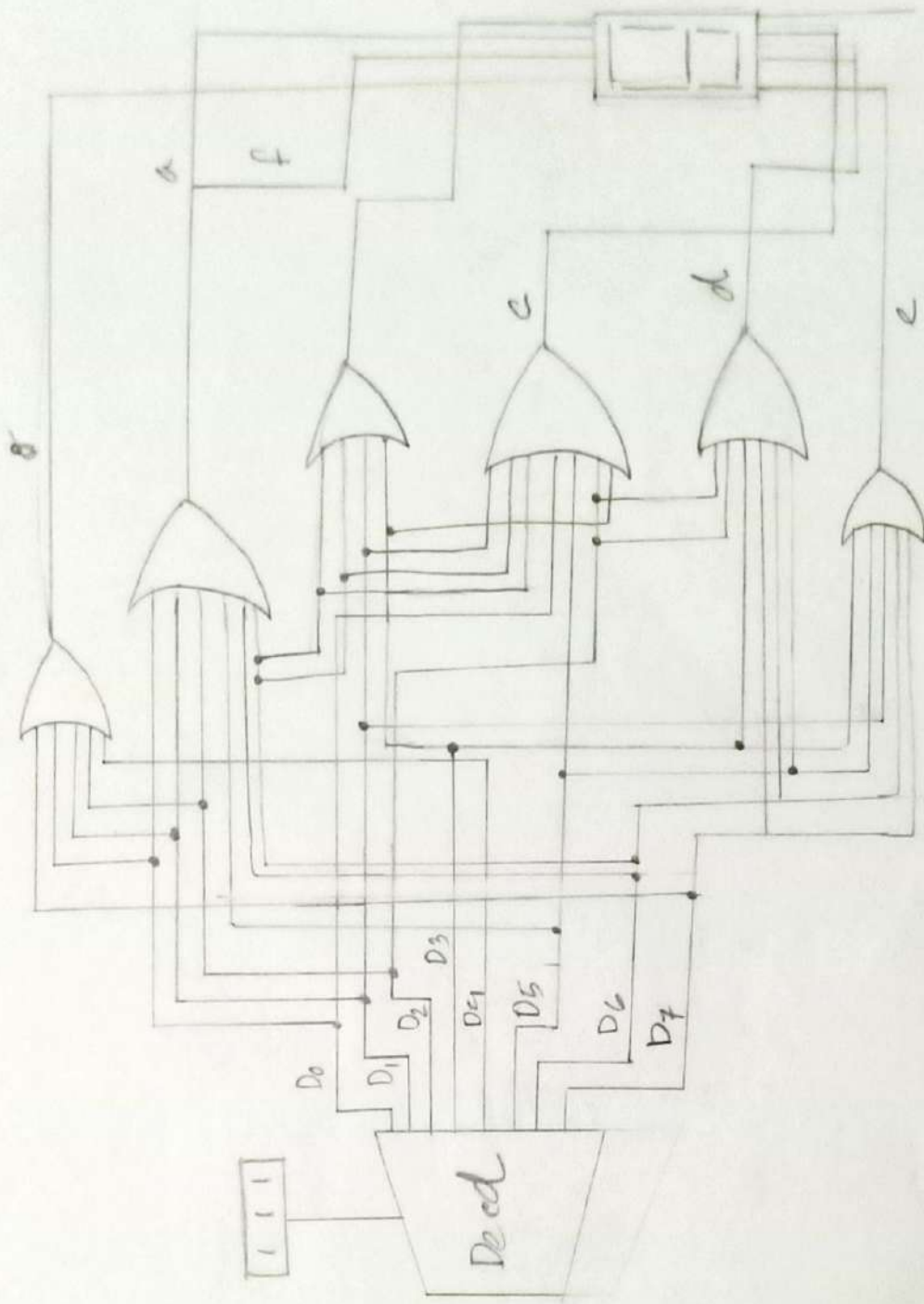


Fig: Generalized SOP Circuit Diagram using Decoder and

OR gate.

Fig: Generalized SOP Multiplexer

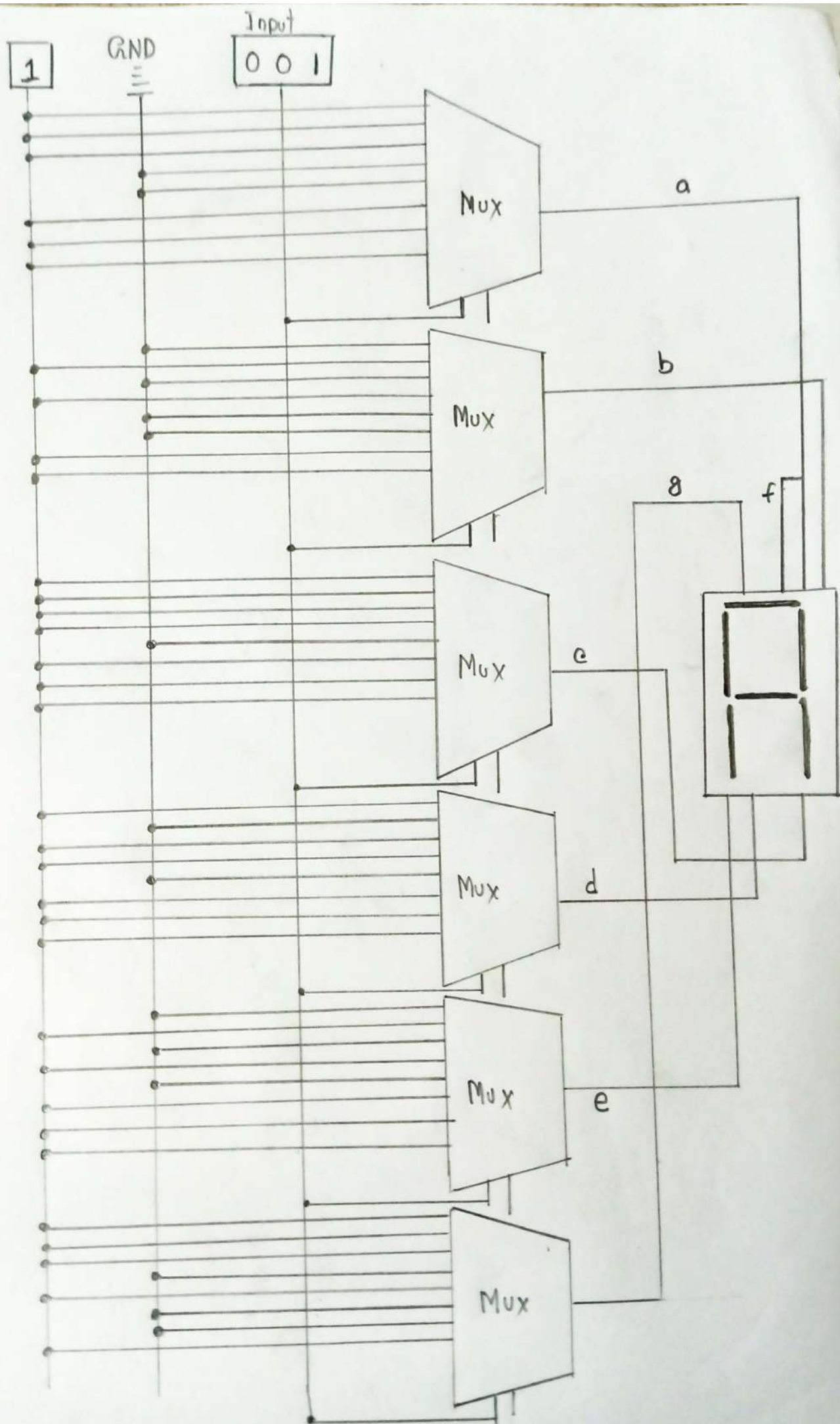

 


Fig. Circuit Diagram For Generalized SOP Equation

PIN	
Facing	South
Output?	No
Data Bus	1
Three state?	No
Pull Behavior	Unchanged
Label	
Label location	West
Label Port	Sanseirif Plain 12

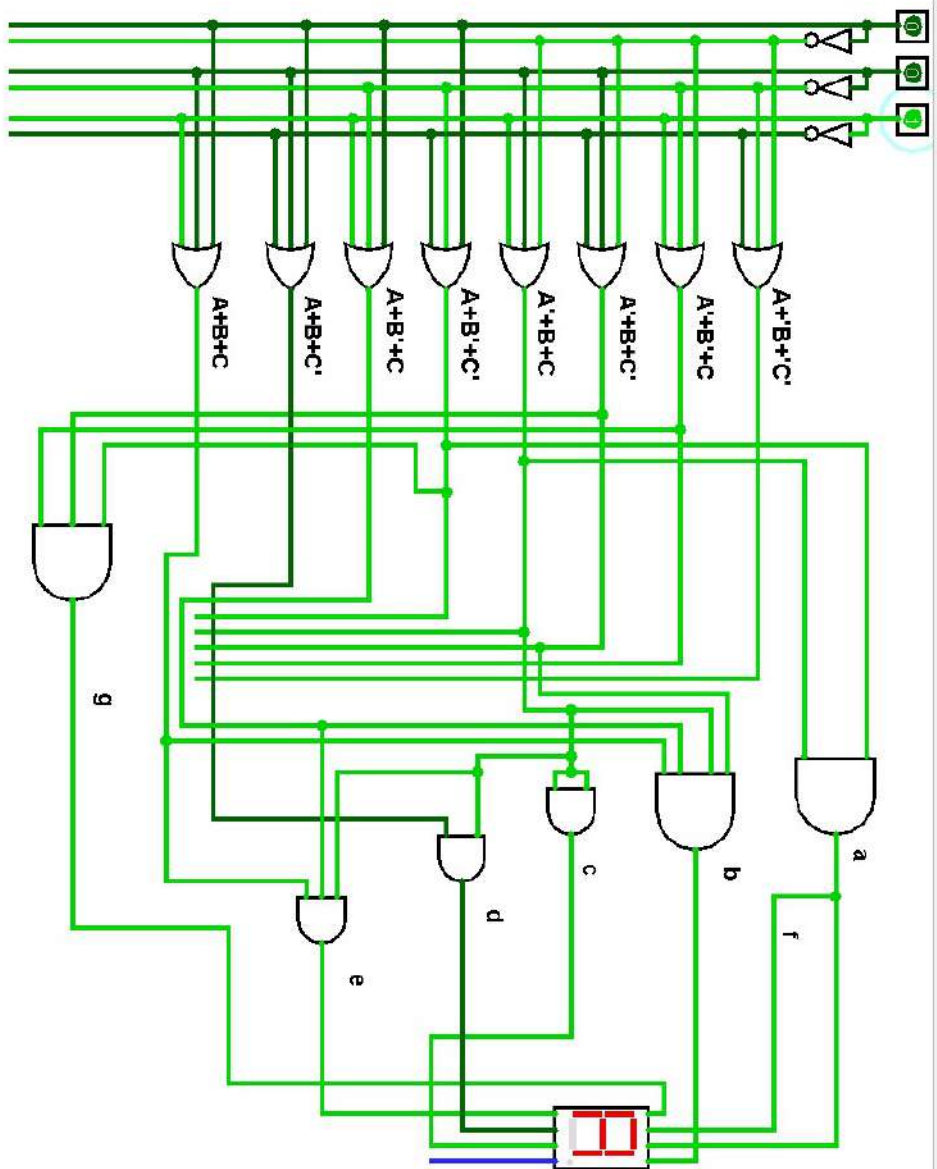


Fig. Circuit Diagram for Simplified SOP Using Basic Gates

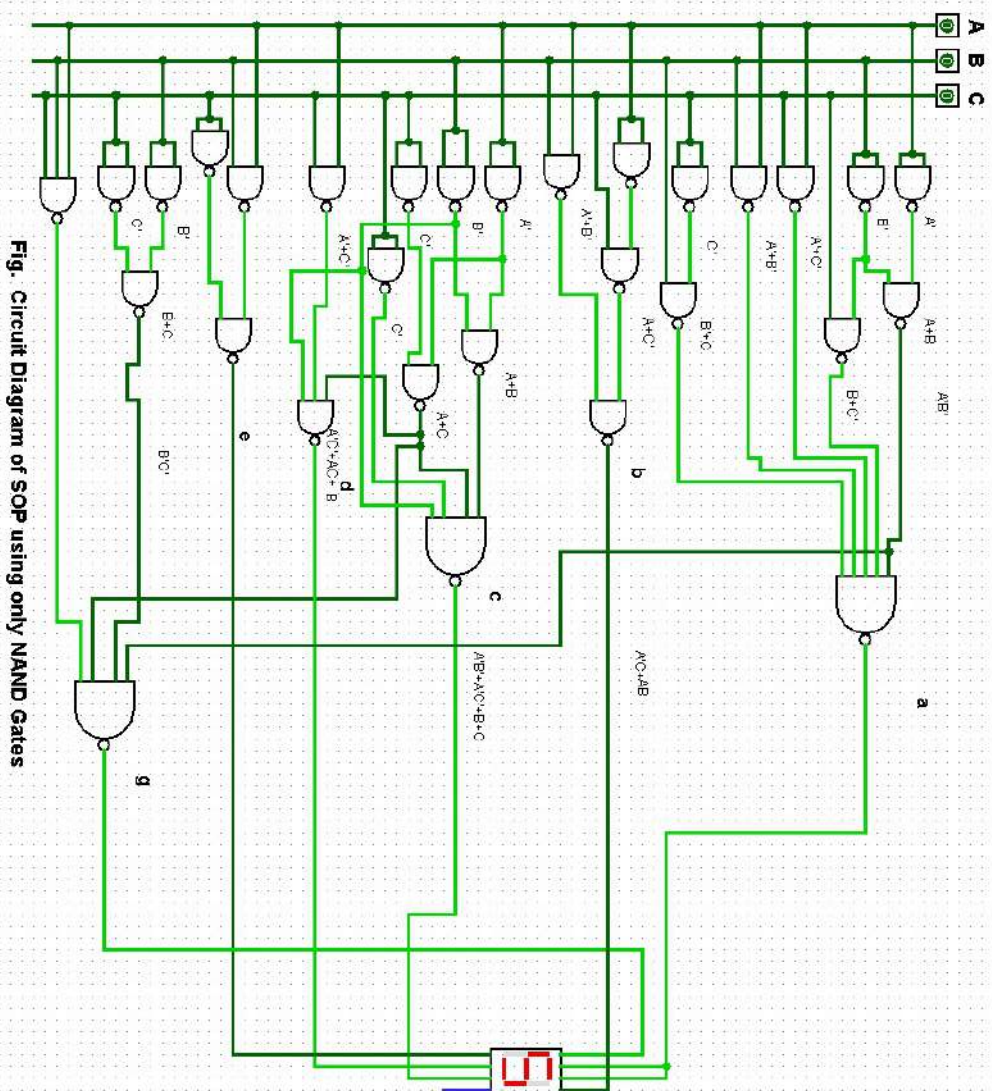


Fig. Circuit Diagram of SOP using only NAND Gates

Circuit: Project-generalized POS	
Circuit Name	Project-Generalized POS
Shared Label	
Shared Label Rating	Fast
Shared Label Font	SansSerif Plain 12

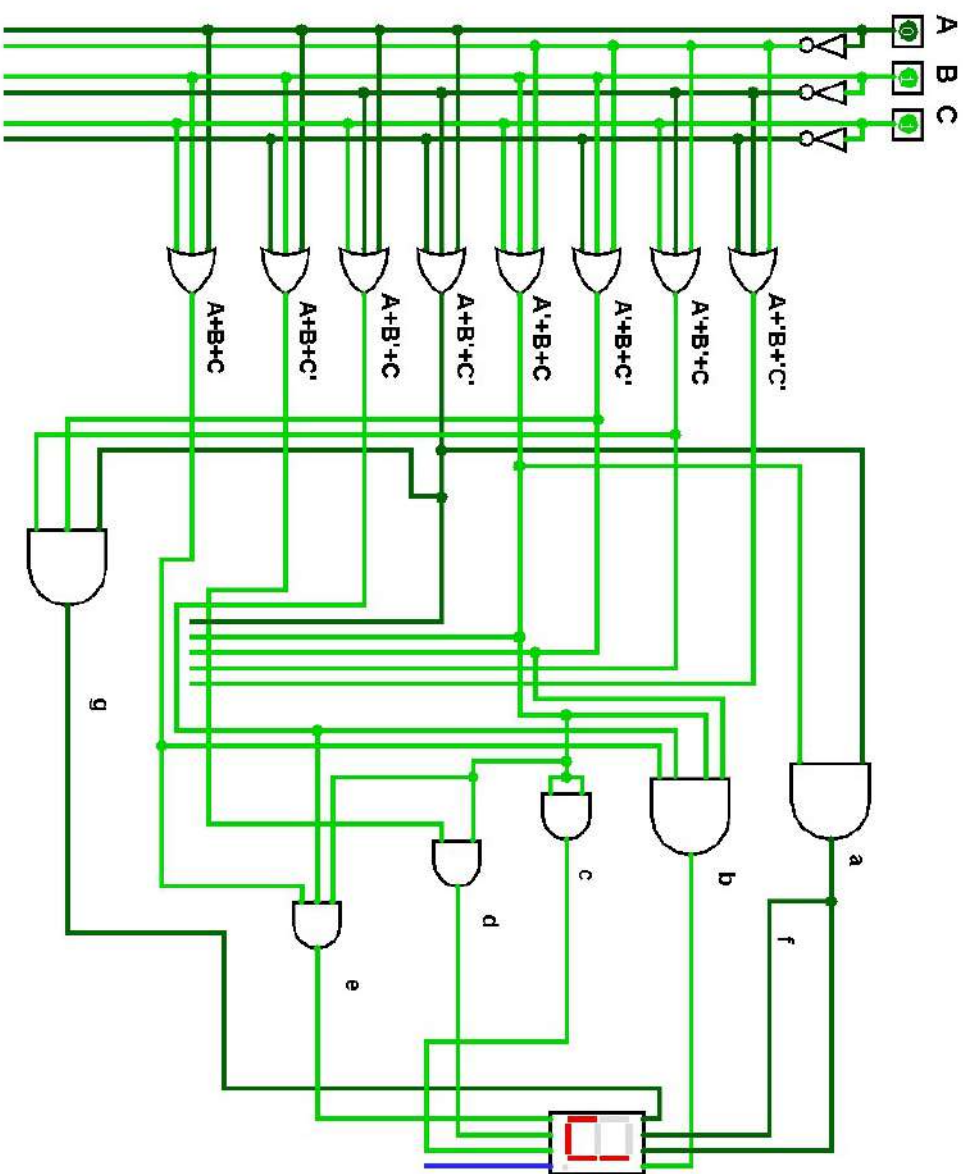


Fig. Circuit Diagram of Generalized POS

Project-Simplified POS*
main
Wiring
Gates
Plexers
Arithmetic
Memory
Input/Output
Base

Circuit Name	main
Shared Label	
Shared Label Ranging	East
Shared Label Font	SansSerif Plain 12

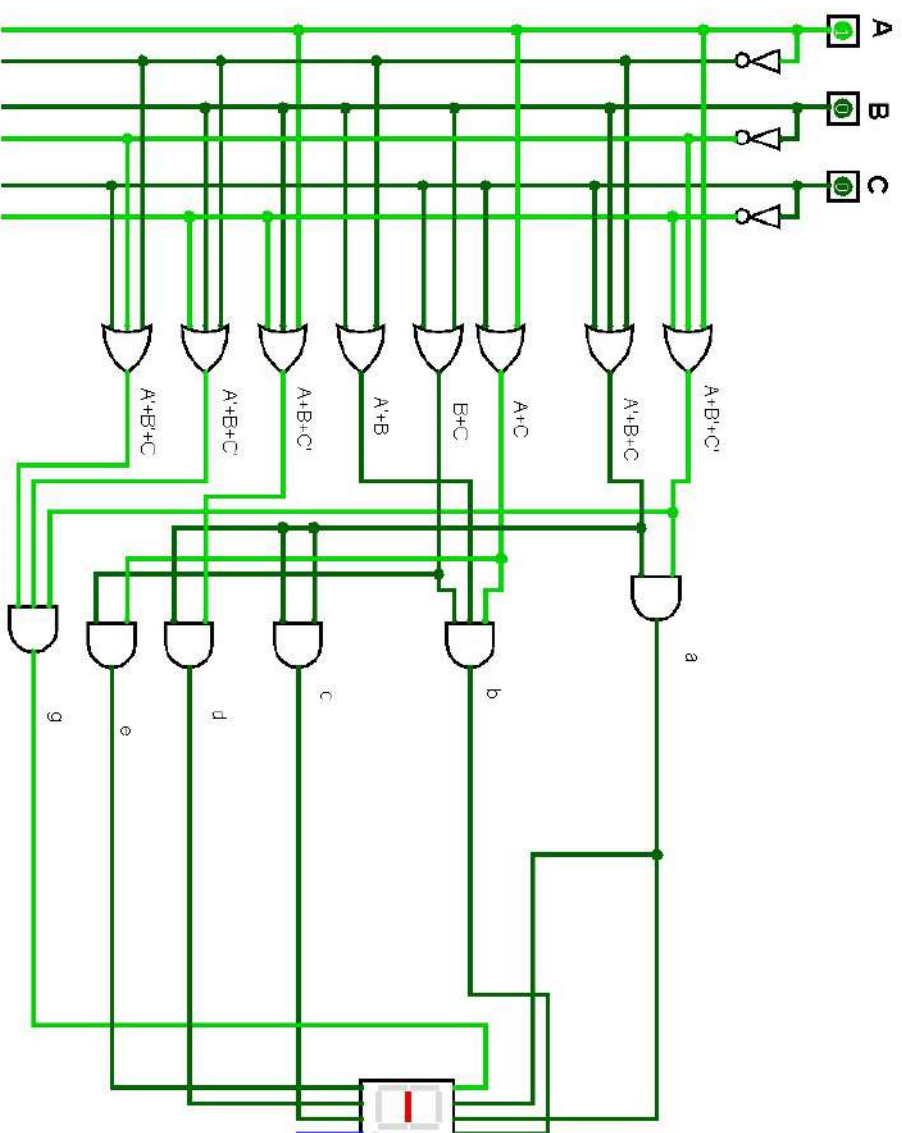


Fig.Circuit Diagram for Simplified POS Using Basic Gates

Circuit: generalized sop using Decoder & OR gates

Circuit Name	Generalized SOP Using Decoder & OR ...
Shared Label	
Shared Label Rating	
Shared Label Font	Standard Plain 12

 


Fig. Generalized SOP Using Decoder and OR Gates

Circuit: Generalized POS Multiplexer	
Circuit Name	Generalized POS Multiplexer
Shared Label	
Shared Label Rating	East
Shared Label Font	SansSerif Plain 12

 


Fig. Generalized SOP Multiplexer

